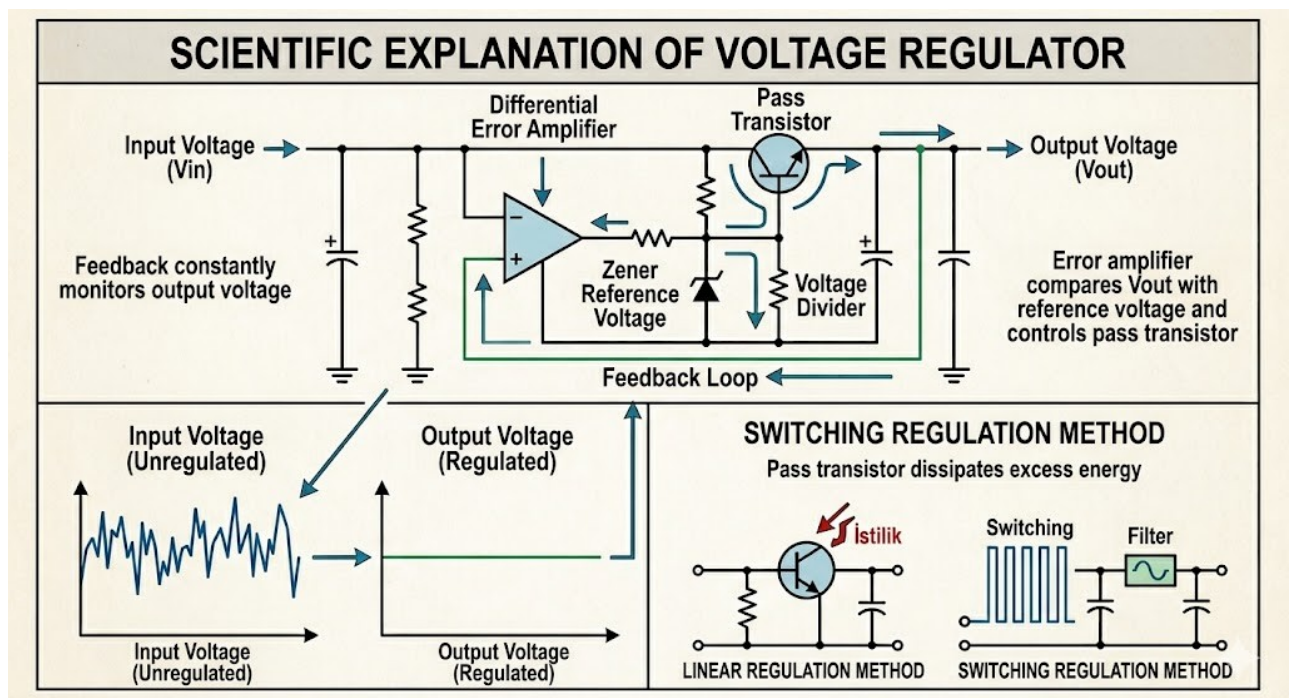


Xumar Bağiyeva, Aysel İsmayılova, Rəşadə Zülfüqarlı, Yasin Quluzade, Ahmed Abdullayev

Verified by: Physics Teacher Azerbaijan Telman Askeraliyev (Fizika Muellimi, Azerbaijan, Baku)



Voltage regulators

A voltage regulator keeps the output voltage stable,
even if the input or load changes.

Topic 1

Voltage

regulation

Topic 2

Linear series

Topic 3

Linear shunt

Topic 4

Switching

- Used in power supplies, phone chargers, and embedded systems.
- Goal: V_{out} stays constant regardless of V_{in} or load changes.

1 / 5

Topic 1

Voltage regulation

How well does the regulator keep V_{out} stable?

$$\text{Regulation} = (V_{\text{no-load}} - V_{\text{full-load}}) / V_{\text{full-load}} \times 100\%$$

- Ideal regulator: 0% — V_{out} never changes.
- Real regulators have a small change — lower % is better.
- Two main problems: load regulation (current changes) and line regulation (input voltage changes).

2 / 5

Topic 2

Basic linear series regulator

A transistor in series controls the output voltage.

Position

Series with load

Control element

Efficiency

Transistor (BJT)

Low (~50%)

- The transistor acts like a variable resistor — it drops extra voltage.
- Simple and clean output — good for low-noise applications.
- Disadvantage: wasted energy becomes heat.

3 / 5

Topic 3

Basic linear shunt regulator

A transistor in parallel (shunt) diverts extra current away.

Position

Parallel with load

Control element

Efficiency

Transistor / Zener

Very low

- Excess current is sent through the shunt transistor, not the load.
- Very simple — Zener diode is the basic version of this.
- Disadvantage: wastes power even when load is small.

4 / 5

Topic 4

Basic switching regulator

Turns the transistor ON/OFF rapidly to control output voltage.

Method

PWM switching

Efficiency

Complexity

High (85-95%)

Higher

- Uses an inductor and capacitor to smooth the switched output.
- Can step up (boost), step down (buck), or invert voltage.
- Used in laptops, phone chargers — anywhere efficiency matters.

Buck (step-down)

Boost (step-up)

Buck-boost (both