

Physics Guide: COMPREHENSIVE TECHNICAL REPORT: OPERATIONAL AMPLIFIERS


Classification: TECHNICAL GUIDE/ EDUCATIONAL

Xumar Bağiyeva, Aysel İsmaylova, Rəşadə Zülfüqarlı, Yasin Quluzade, Ahmed Abdullayev

Verified by: Physics Teacher Azerbaijan Telman Askeraliyev (Fizika Muellimi, Azerbaijan, Baku)

ANALYTICAL FOUNDATIONS OF OPERATIONAL AMPLIFIERS

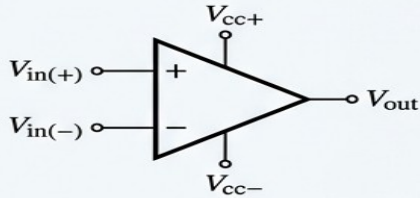1 IDEAL CHARACTERISTICS & DIFFERENTIAL GAIN ANALYSIS



Open-Loop Gain:

$$A_{OL} = A_{OL} \frac{V_{in}}{R_1}$$

Differential Input:


$$V_{id} = V_{in(+)} - V_{in(-)}$$

Ideal:


- Infinite Gain ($A_{OL} = \infty$)
- Infinite Input Impedance ($R_{in} = \infty$)
- Zero Output Impedance ($R_{out} = 0$)

2 THE FUNDAMENTAL OPERATING RULES

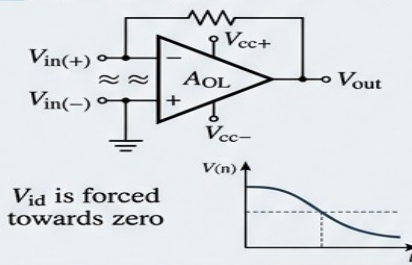1 The Virtual Ground Concept (with Negative Feedback)




2 Zero Input Current

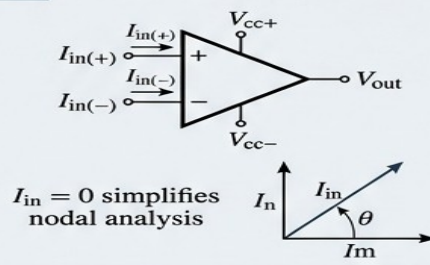

3 APPLICATION OF THE GOLDEN RULES

INVERTING AMPLIFIER ANALYSIS

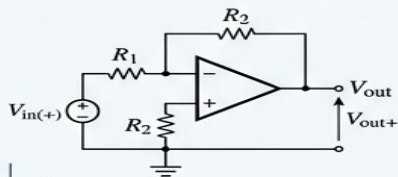

Nodal equations:

$$V_{id} = V_{in} + V_{dif} = V_{id}$$


$$V_{id} = V_{in(+)} - V_{in(-)} + V_{in(-)}$$

$$A_V = -\frac{R_2}{R_1}$$

Predict	Actuals
A_L	≥ 1
A_{L+}	$< \text{erad}$

Gain	Actual
$A_V =$	$-\frac{R_2}{R_1}$

NON-INVERTING AMPLIFIER ANALYSIS

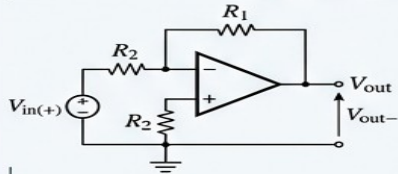

Nodal equations:

$$V_{id} = V_{in(+)} - V_{in(-)} = R_2$$

$$V_{id} = -R_{in(+)} + V_{in(-)} + R_2$$

$$A_V = 1 + \frac{R_2}{R_1}$$

Predict	Actuals
A_1	No
R_2	No

Gain	Actual
$A_V =$	$1 + \frac{R_2}{R_1}$

K - Legend LfX - Times New Roman
Vid - Times New matasr Vout - operational amplifiers

An **Operational Amplifier (Op-Amp)** is a high-gain, direct-coupled, electronic voltage amplifier with differential inputs and, usually, a single-ended output. It is the fundamental building block of analog signal processing circuits.

- **Differential Inputs (V_{in+} and V_{in-}):** The op-amp amplifies the *difference* between two input voltages. The **Non-Inverting Input (V_{in+})** keeps the output in phase, while the **Inverting Input (V_{in-})** flips the output phase by 180° .

- High Open-Loop Gain (A_{OL}):** An ideal op-amp has infinite gain, meaning even a tiny voltage difference between the two inputs will violently drive the output to its maximum limit.
- The Feedback Loop:** To make the amplifier useful and predictable, a portion of the output signal is fed back into the inverting input (V_-). This **Negative Feedback** tames the massive gain, stabilizes the circuit, and allows engineers to set exact amplification factors using external resistors.
- Virtual Ground Concept:** In a closed negative feedback loop, the op-amp will do everything it can to make the voltage at both input terminals equal ($V_+ = V_-$). If one pin is tied to ground (0V), the other pin acts as a "virtual ground," holding a potential of 0V without being physically wired to the ground rail.

III. SECTION 2: IDEAL VS. REAL OP-AMP CHARACTERISTICS

When designing circuits in tools like Proteus or Tinkercad, engineers must balance the mathematical rules of an "ideal" op-amp against the physics of a physical silicon chip (like the classic **UA741** or **LM358**).

Parameter	Ideal Op-Amp	Real Op-Amp (Typical)	Impact on Circuit
Input Impedance (Z_{in})	Infinite (∞)	$2\text{ M}\Omega$ to $10^{12}\text{ }\Omega$	Zero Current Draw: Ideal inputs draw absolutely no current, preventing loading effects on preceding sensor stages.
Output Impedance (Z_{out})	Zero ($0\text{ }\Omega$)	$10\text{ }\Omega$ to $100\text{ }\Omega$	Maximum Power Transfer: Low output resistance ensures it can drive heavy loads without dropping voltage.
Open-Loop Gain (A_{OL})	Infinite (∞)	$100,000$ to $200,000$	Determines how accurately the negative feedback loop can control the overall system behavior.
Bandwidth (BW)	Infinite (∞)	From 1 MHz to a	Real op-amps lose their ability to amplify cleanly as the signal

Parameter	Ideal Op-Amp	Real Op-Amp (Typical)	Impact on Circuit
		few GHz	frequency goes up.

✂ SECTION 3: KEY CONFIGURATIONS & APPLICATIONS

By changing how resistors are wired around the feedback loop, an op-amp can perform various mathematical and signal conditioning operations:

1. Inverting Amplifier

- **Design:** The input signal is fed through a resistor into the inverting terminal (V_-), while the non-inverting terminal (V_+) is grounded.
- **Application:** It scales the amplitude of the input signal up or down while reversing its electrical polarity.

2. Non-Inverting Amplifier

- **Design:** The input signal connects directly to the non-inverting terminal (V_+), and the feedback network goes to the inverting terminal (V_-).
- **Application:** Used when high input impedance is mandatory, allowing you to amplify weak sensor voltages without distorting or loading the sensor circuit.

3. Voltage Follower (Buffer)

- **Design:** The output pin is tied directly back into the inverting input pin (V_-) with a direct wire (100% feedback), and gain equals exactly 1.
- **Application:** It acts as an isolation buffer. It isolates a sensitive signal source (like an LDR voltage divider) from a heavy load down the line, preserving signal integrity.